



Echem Rnx. Engg. CL 611

Prof. Bharat Suthar

Department of Chemical Engineering
IIT Bombay, Mumbai, India, 400076

Basics of EIS

bharat.k.suthar[at]iitb.ac.in

Landline: +91 (22) 2576 7243

Admin:





- ☐ Reminder:
 - ☐ Start working on the projects

Outline



- ☐ Motivation for EIS
- ☐ Impedance (loosely defined)
 - ☐ Resistance
 - ☐ Capacitance (double layer capacitance)
 - ☐ Inductance (not covered)
- ☐ Impedance: definition
- ☐ Examples




Workings of a Li-ion Battery

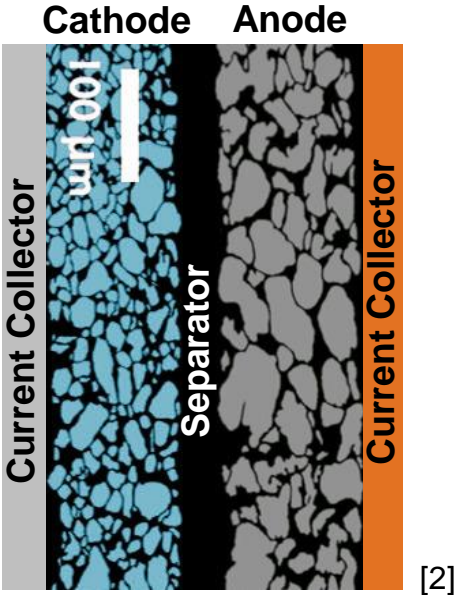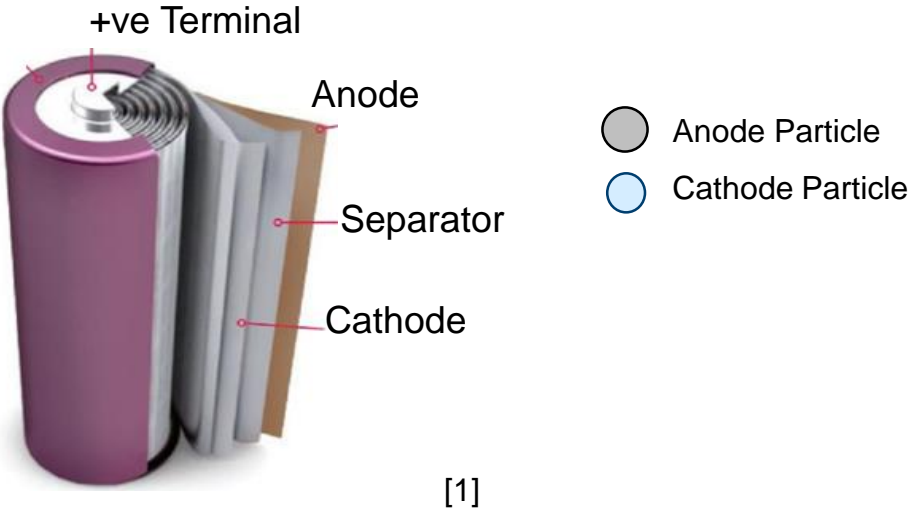

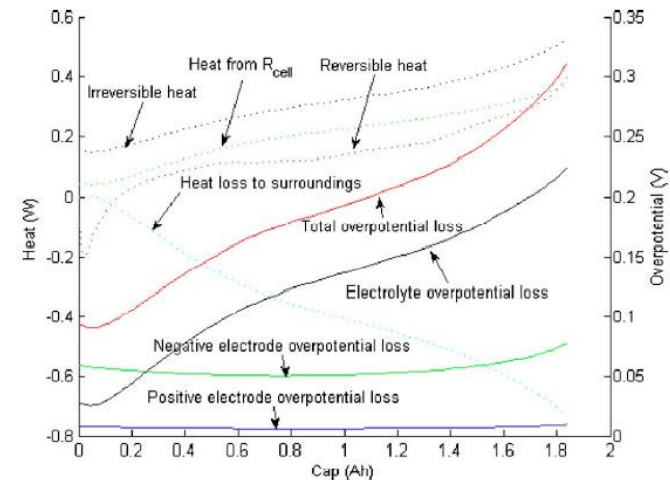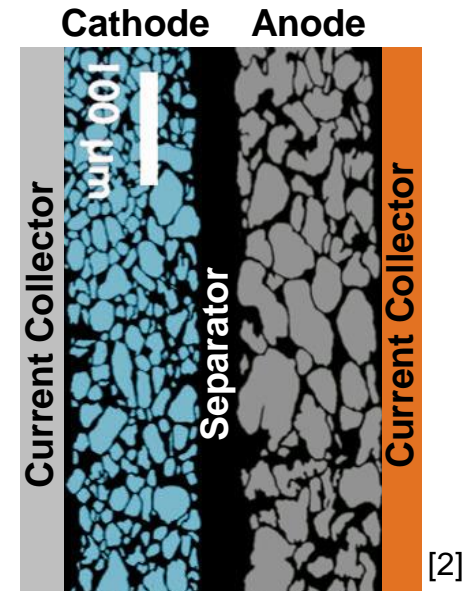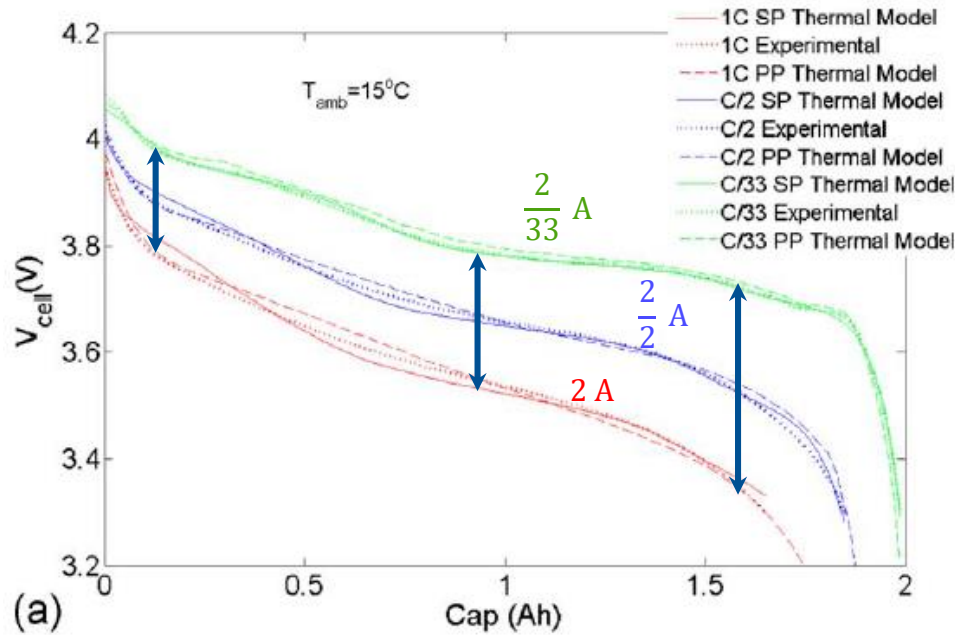1. Image: Miller, *Johnson Matthey Technol. Rev.*, (2015).
 2. Image: Smith et al., *J. Electrochem. Soc.*, (2009).

EIS: Motivation



Quantification of various resistance in batteries (dynamic system)



Guo, Meng, Godfrey Sikha, and Ralph E. White. *JES* 158.2 (2010): A122.

EIS: Motivation

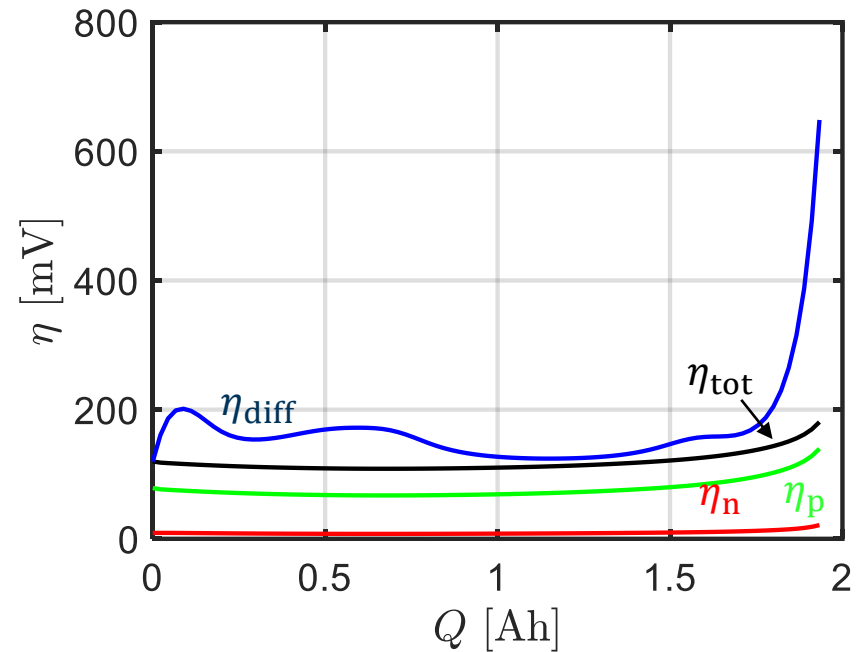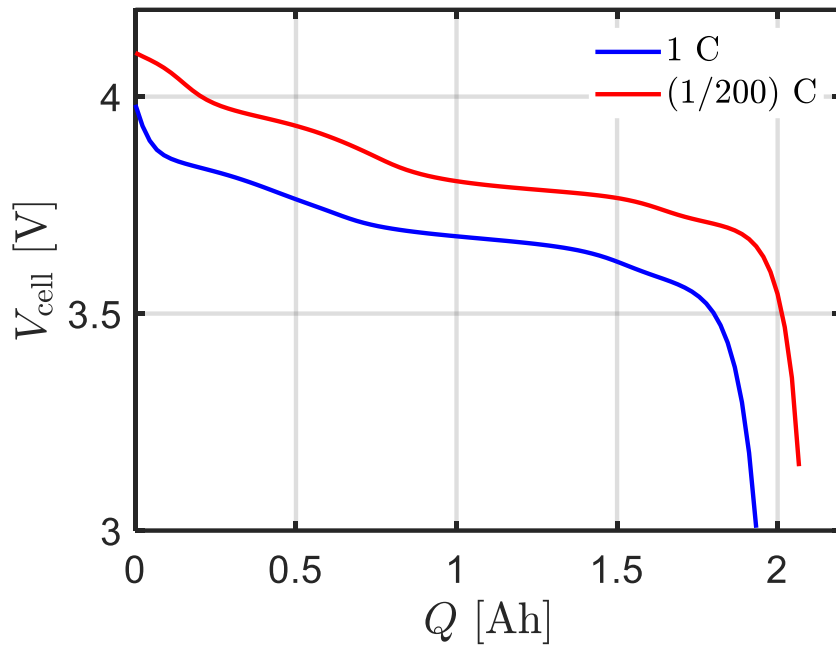Quantification of various resistance in batteries (dynamic system)




Guo, Meng, Godfrey Sikha, and Ralph E. White. *JES* 158.2 (2010): A122.

EIS: Motivation



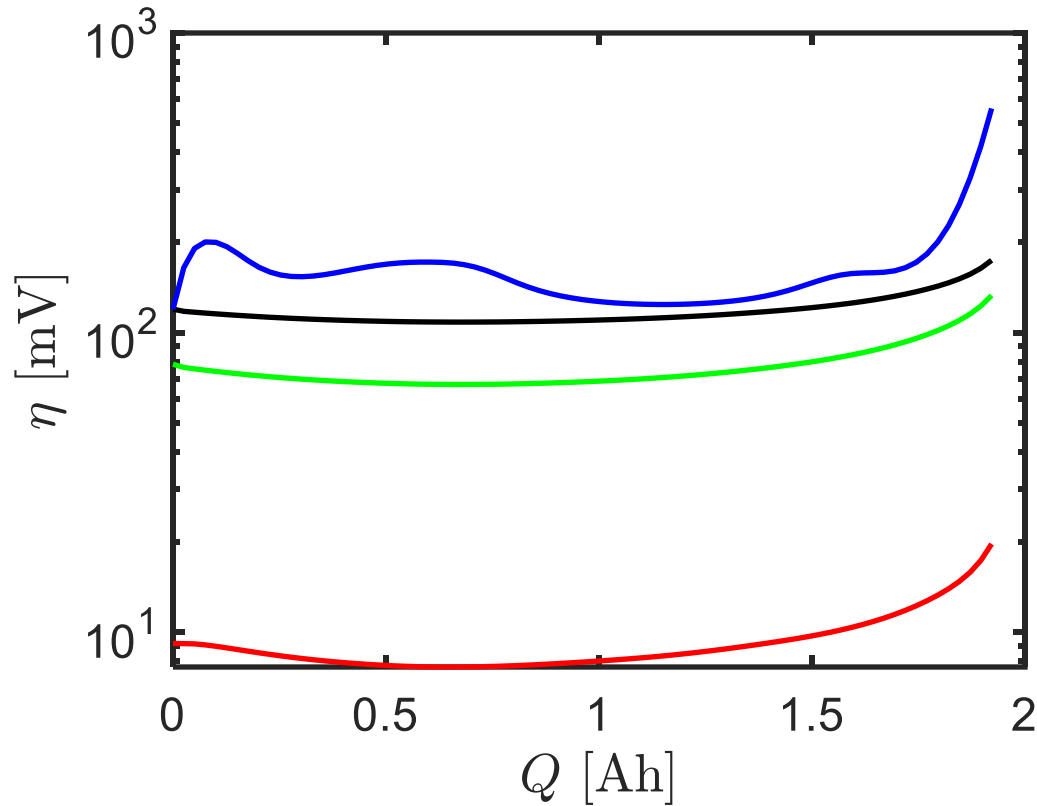Quantification of various resistance in batteries (dynamic system)





Guo, Meng, Godfrey Sikha, and Ralph E. White. *JES* 158.2 (2010): A122.


EIS: Motivation



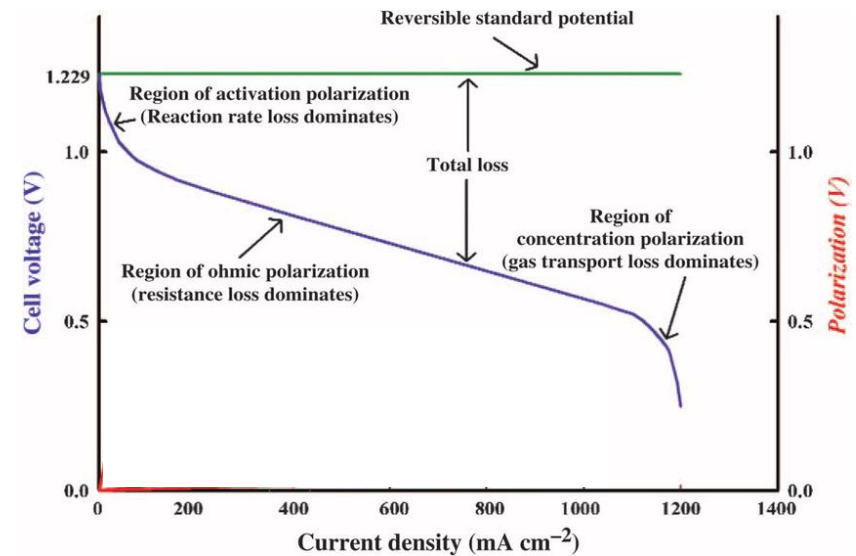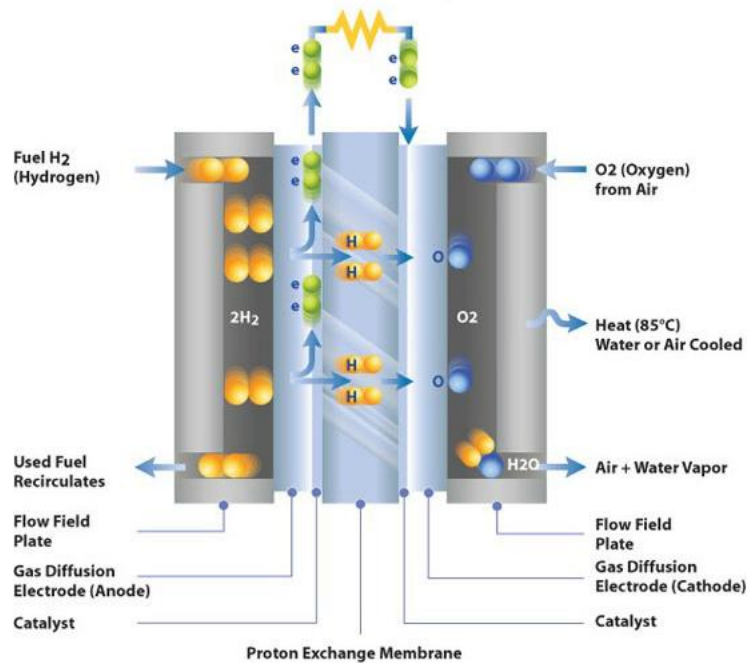Quantification of various resistance in fuel cell and electrolyzers (steady state systems)



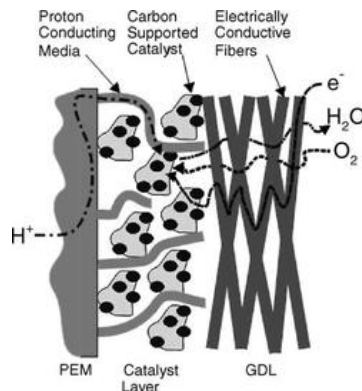Zhang, Jintao+ " *Science advances* 1.7 (2015): e1500564.






https://en.wikipedia.org/wiki/Membrane_electrode_assembly

Outline



- ☐ Motivation for EIS
 - ☐ Previous encounter
- ☐ Impedance (loosely defined)
 - ☐ Resistance
 - ☐ Capacitance (double layer capacitance)
 - ☐ Inductance (not covered)
- ☐ Impedance: definition
- ☐ Examples


Previous Encounter: Process Control

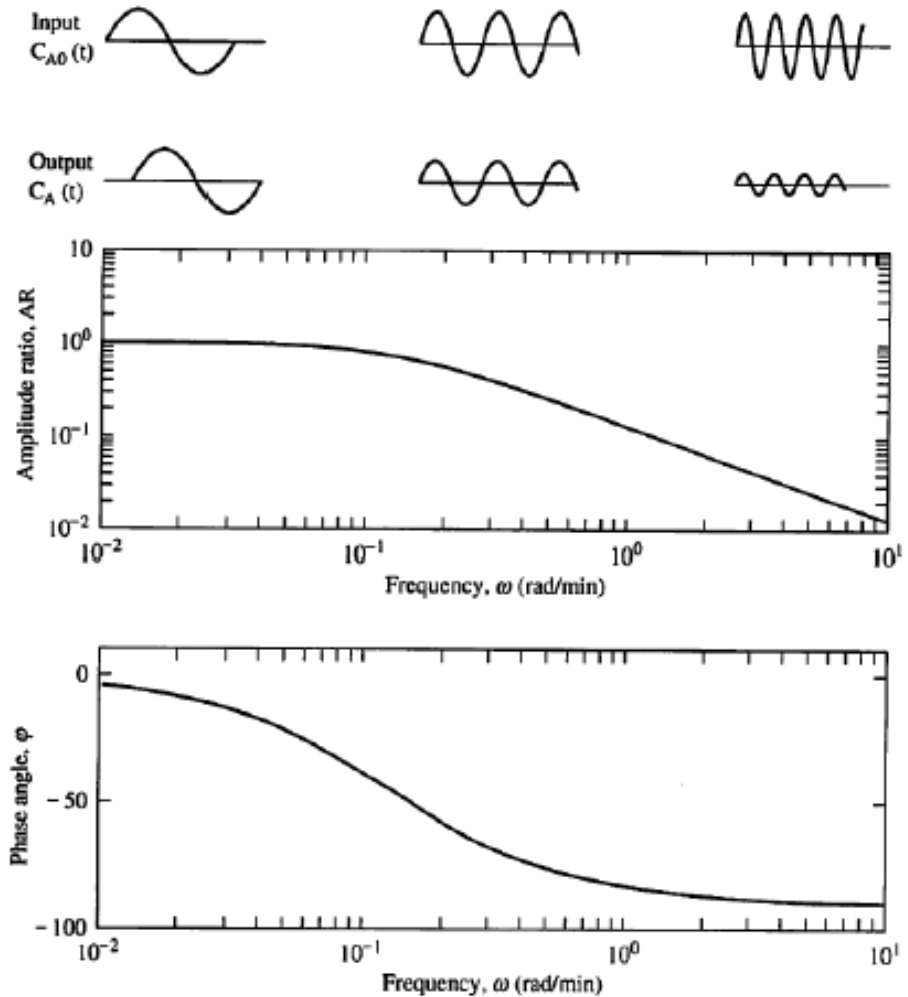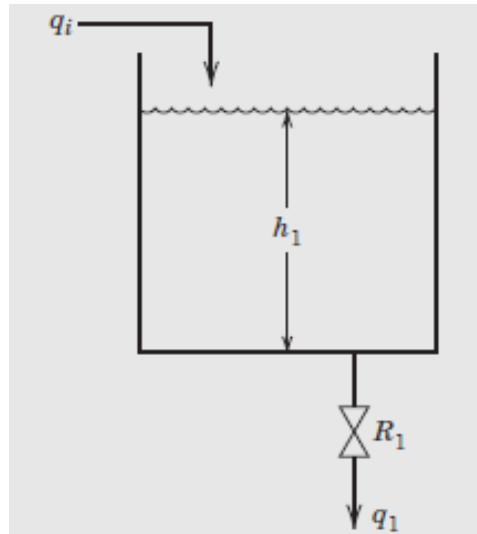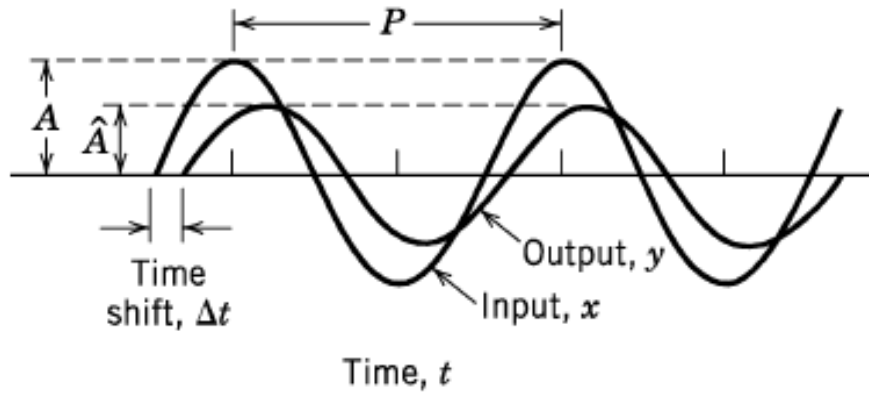

Previous Encounter: Process Control



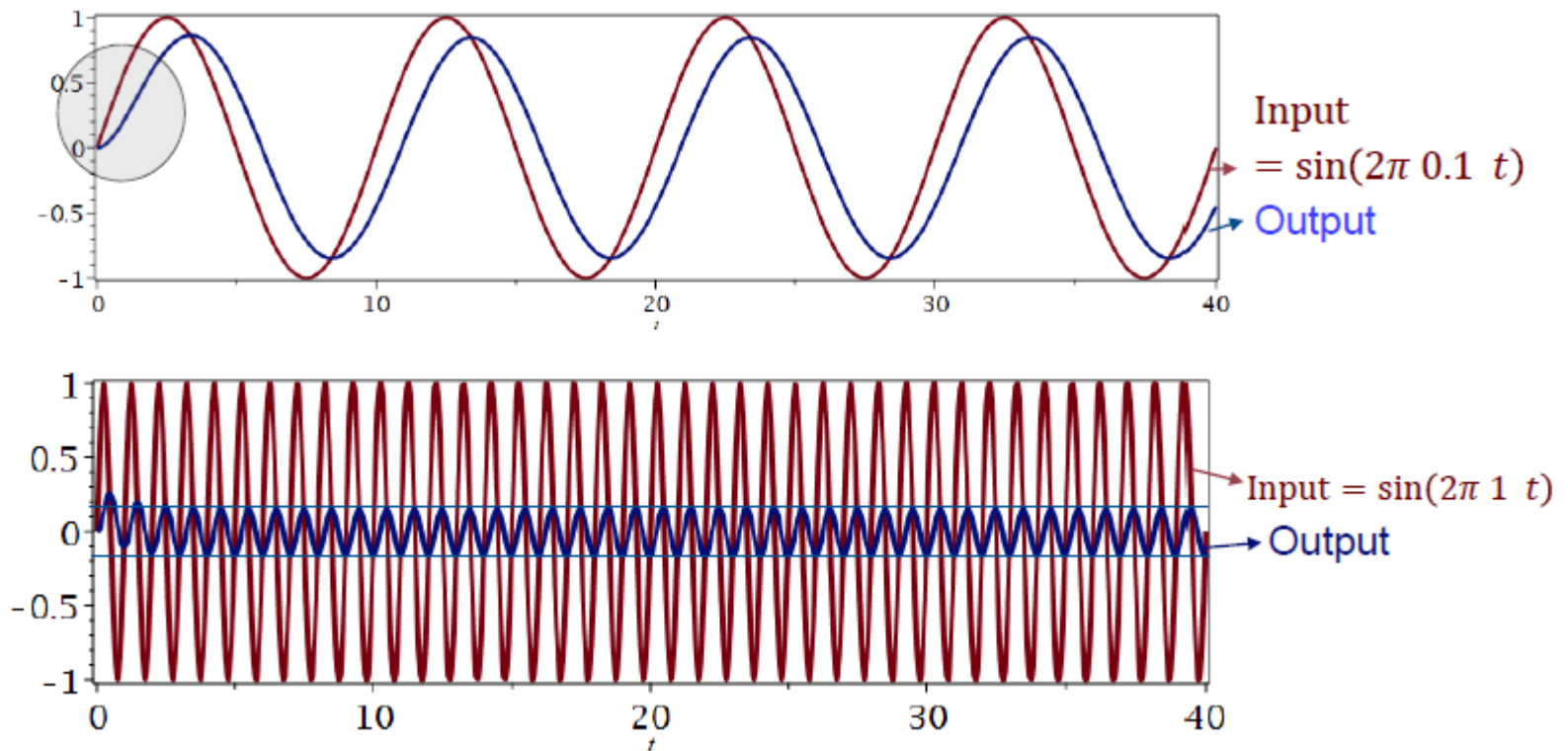- ❑ Comparison of two difference frequencies for tank height control problem.




Outline



- ☐ Motivation for EIS
 - ☐ Previous encounter
- ☒ Impedance (loosely defined)
 - ☒ Resistance
 - ☒ Capacitance (double layer capacitance)
 - ☒ Inductance (not covered)
- ☐ Impedance: definition
- ☐ Examples

What is impedance?



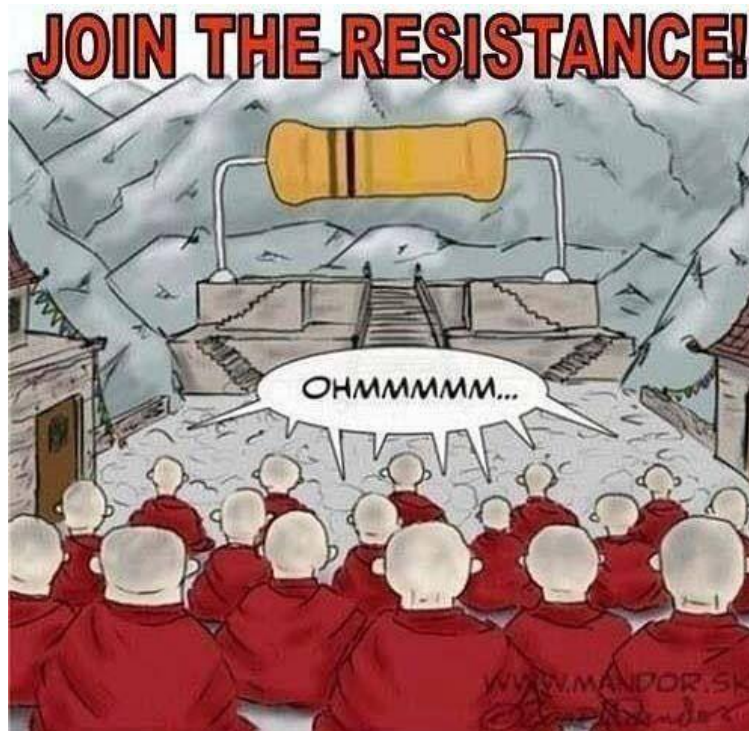
- ❑ Generalization of the concept of resistance:
- ❑ Purpose of EIS:
 - ❖ Measure transport and kinetic and (possibly thermodynamic) parameters of the underlying systems.



Resistances are Everywhere ☹️




- Resistance → Loosely speaking → Measure of **opposition to the flow** of “xyz”
- Electrical Resistance
 - Potential drop (measure of opposition) to the flow of electric current (**Ohm's Law**)
- Transport Resistance
 - Charge Transport
 - Potential drop to the flow of ionic/diffusive current
 - Neutral Mass/Momentum Transport
 - Pressure drop to the flow of diffusion/convective (e.g. **Darcy's Law, Newton's Law of Viscosity**)
 - Thermal
 - Temperature drop to the flow of heat current (**Fourier's law**)
- Kinetic Resistance
 - Potential drop to the flow of reaction current

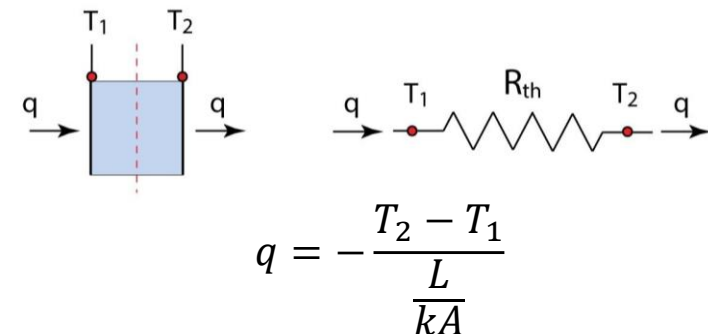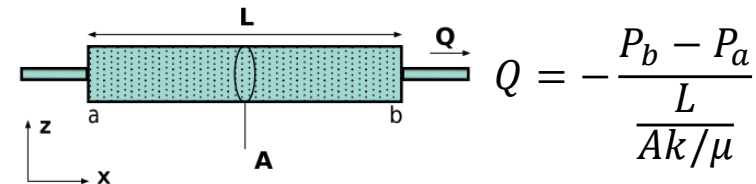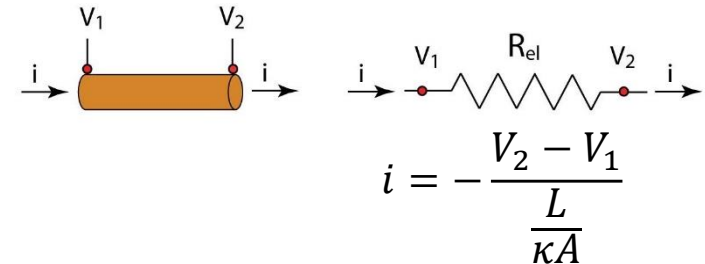

Resistance


$$I = \frac{\Delta V}{R}$$

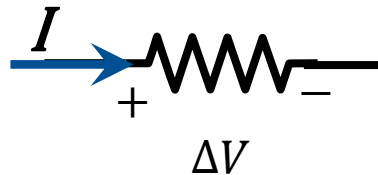- ❑ Current and voltage drop are directly proportional!
- ❑ There is no dynamics between ΔV and I
 - ❖ i.e. algebraic relation
- ❑ Current and voltage has no phase difference.




- ❑ A resistance will let the current pass through it for a fixed potential difference ΔV

Examples of Resistances:

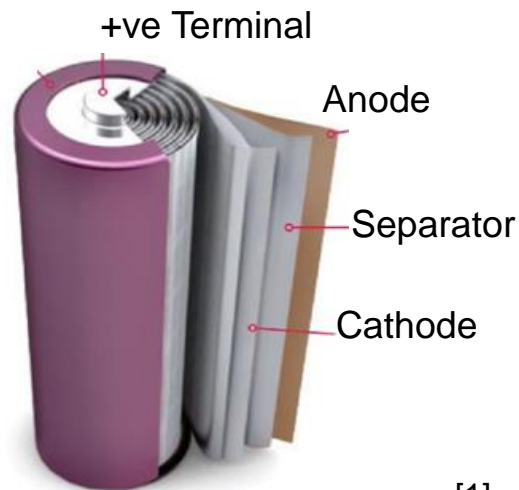

[1]

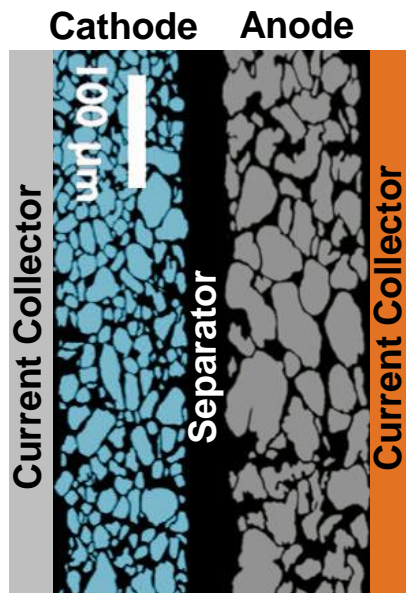

[2]

- ☐ Resistance of metal wire
- ☐ Resistance of a current collector
 - ❖ Provided the inductance is not considered.
- ☐ Electric resistance of porous electrode
- ☐ Solution resistance in a separator
 - ❖ When only migration is present (conductivity based resistance)
 - ❖ What happens when conc. Gradient is present.
- ☐ Solution resistance of the porous electrode
 - ❖ Due to limited conductivity in the electrolyte residing in the pores.
 - ❖ What happens when conc. gradient is present.



1. Image: Miller, *Johnson Matthey Technol. Rev.*, (2015).
2. Image: Smith et al., *J. Electrochem. Soc.*, (2009).

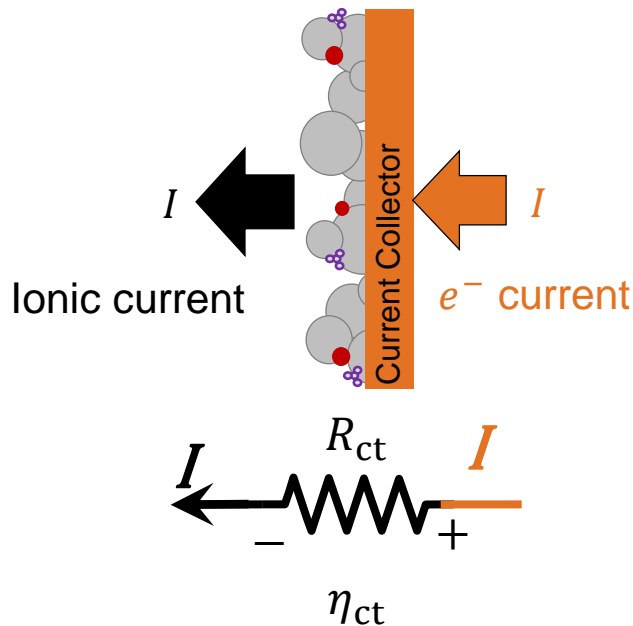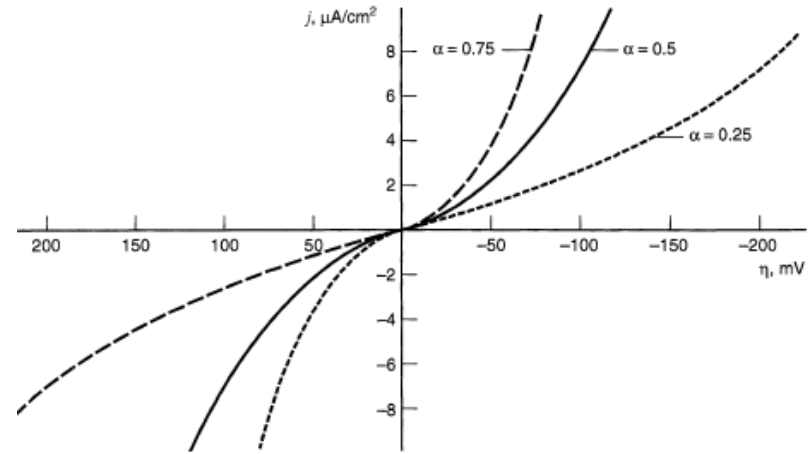Example: Charge Transfer Resistance



□ Charge transfer resistance:

- ❖ Nonlinear resistance
- ❖ I-V curve of normal resistance vs Butler-Volmer (BV) kinetics
- ❖ Derivation of R_{ct} for BV (what is η)




$$\begin{aligned}
 i &= i_0(e^{-\alpha f \eta} - e^{(1-\alpha) f \eta}) \\
 i &= i_0(1 - \alpha f \eta - (1 + (1 - \alpha) f \eta) + \text{HOD}) \\
 i &= i_0(-f \eta) \\
 i &= -f \eta i_0 \\
 i &= -\frac{\eta}{\left(\frac{1}{f i_0}\right)} \\
 R_{ct} &= \frac{RT}{F i_0}
 \end{aligned}$$


Linear Resistance vs BV



□ Linear resistance:

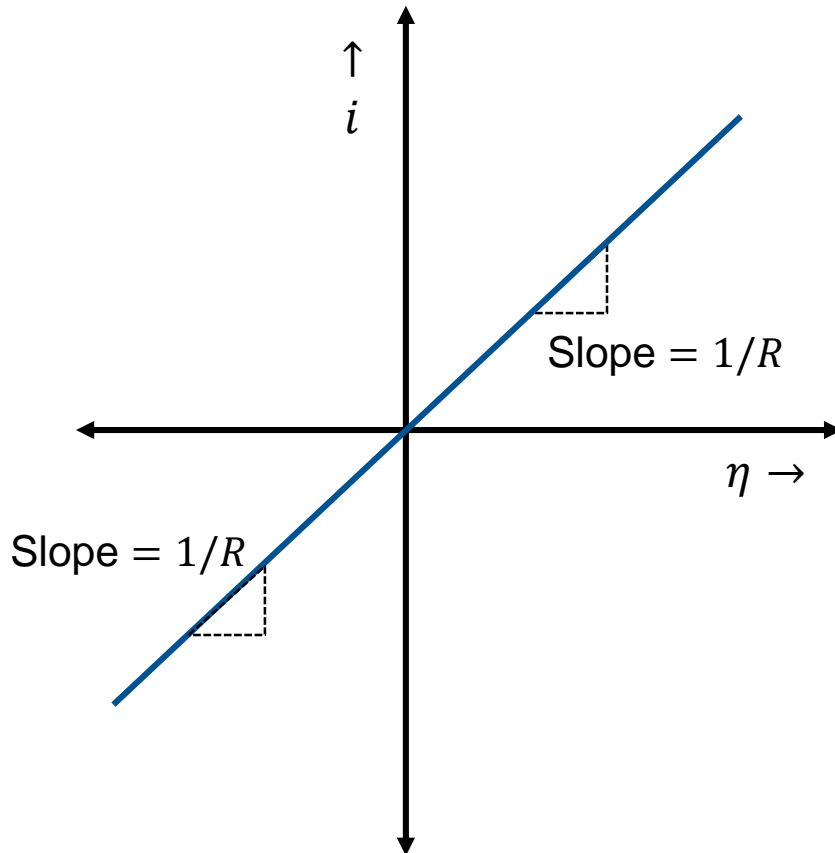


□ Butler-Volmer:

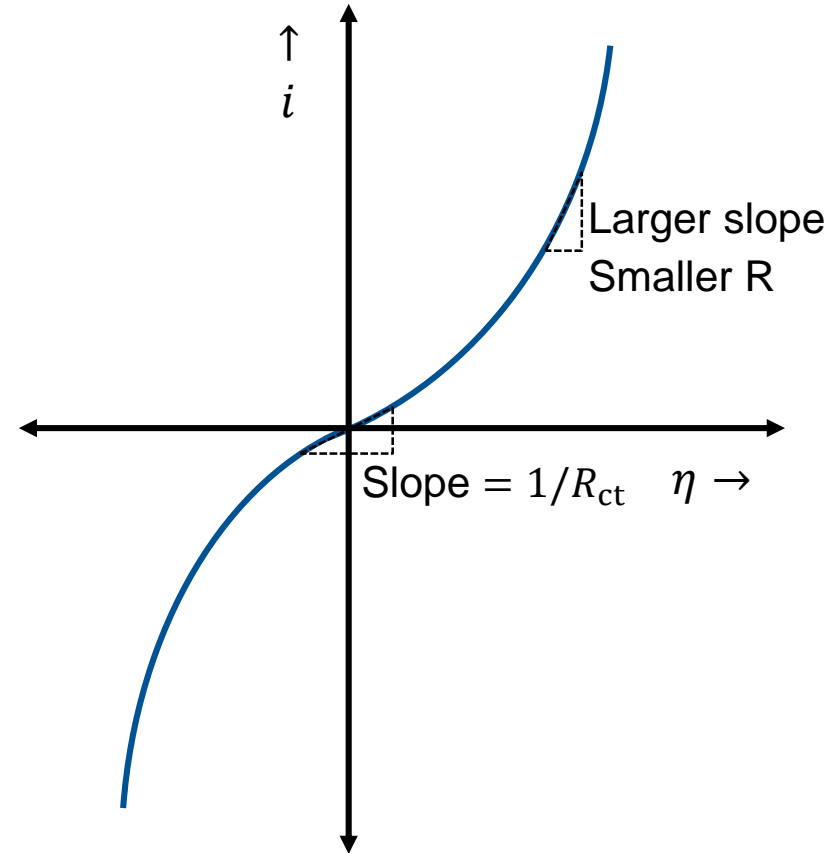

Nice Properties of Resistances

They follow series and parallel rule!

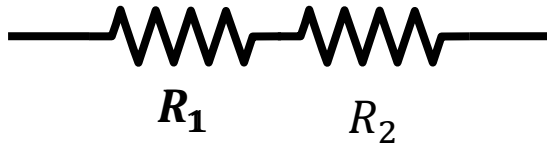


$$R_{\text{sys1}} = R_1 + R_2$$



$$\text{If } R_1 = R_2$$

$$R_{\text{sys1}} = 2R$$

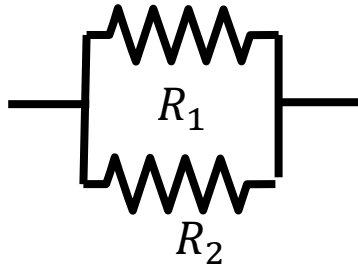

$$R_{\text{sys2}} = \frac{R_1 \times R_2}{R_1 + R_2}$$





$$\text{If } R_1 = R_2$$

$$R_{\text{sys2}} = \frac{R}{2}$$

Charge conservation in electrochemical systems

□ Approximation of electroneutrality

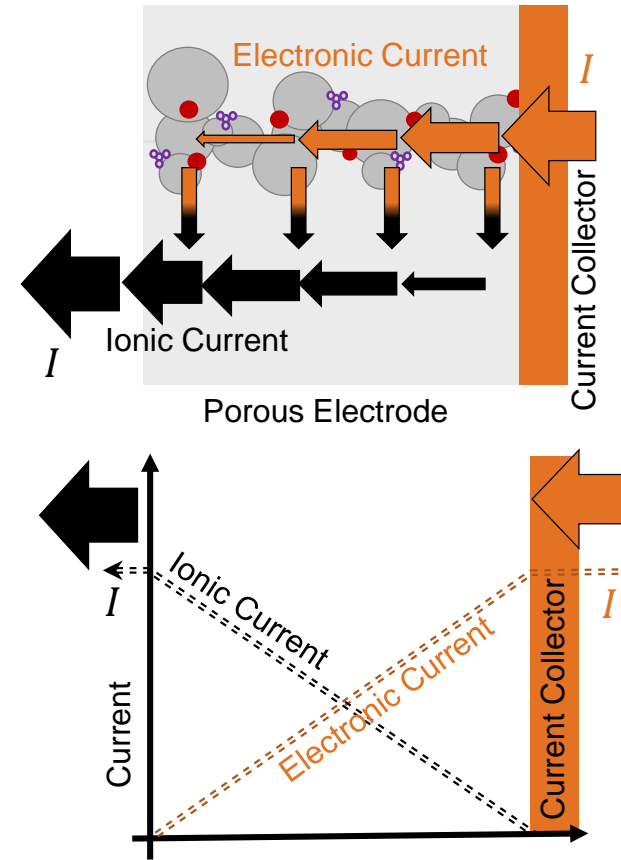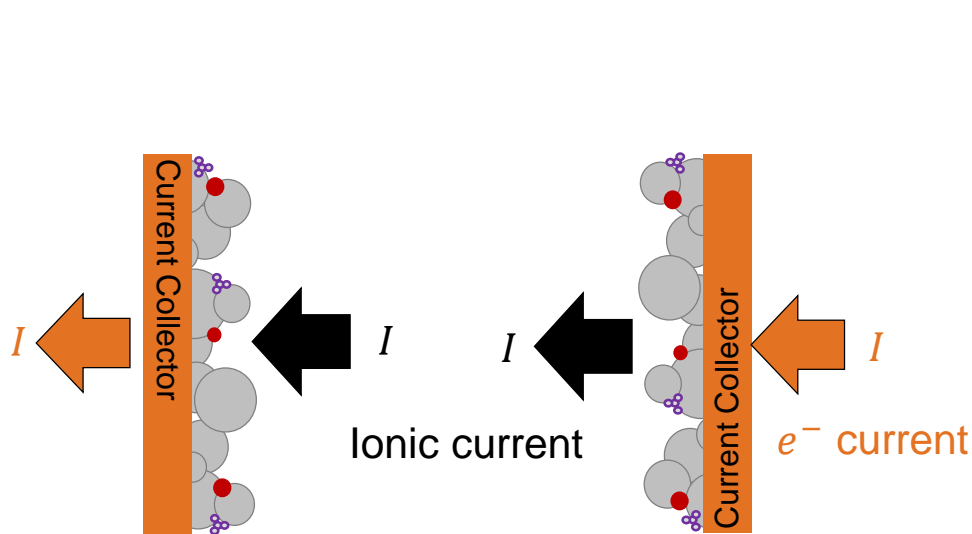


Outline



- ☐ Motivation for EIS
 - ☐ Previous encounter
- ☐ Impedance (loosely defined)
 - ☐ Resistance
 - ☒ Capacitance (double layer capacitance)
 - ☐ Inductance (not covered)
- ☐ Impedance: definition
- ☐ Examples

Analogy: Capacitor

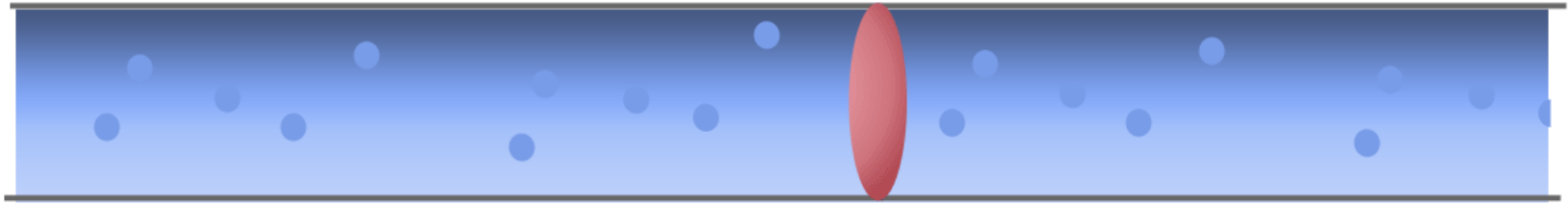

- **Capacitor is not leaky**
- **Capacitor can not let the constant current pass**
- **Capacitor stores energy!**

The problem with analogy is that in the end they are always wrong!



Ceramic Capacitor vs DL Capacitor



❑ Double layer capacitor

❑ Capacitance with dielectric
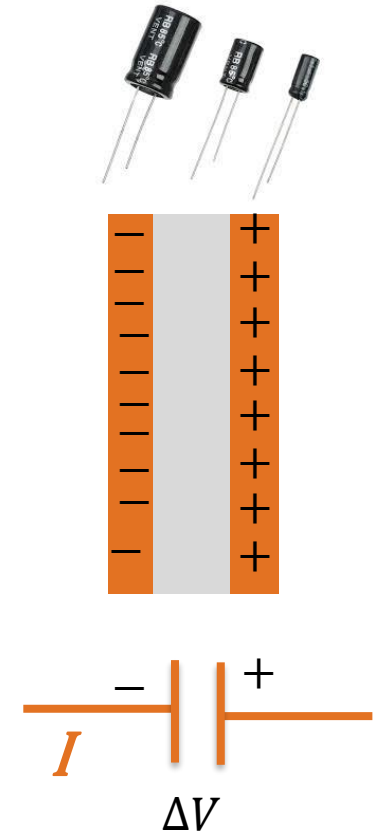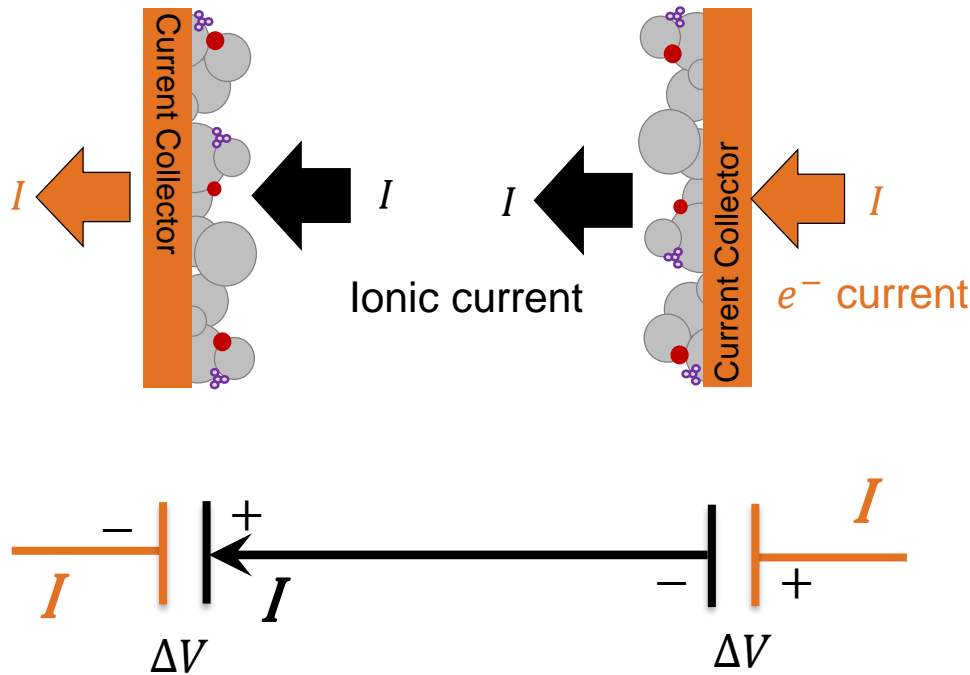
$$C = \epsilon \left(\frac{A}{d} \right)$$



Current vs Diffusive Flux



□ Explanation:


Resistances are insufficient

to describe capacitor behavior

Resistances vs Capacitance


Electrical Resistance

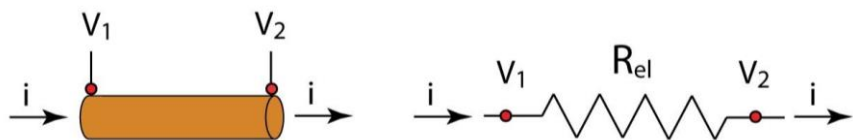- Potential drop (measure of opposition) to the flow of electric current (**Ohm's Law**)




$$i = -\frac{1}{R_{el}} V_2 - V_1 = -\frac{1}{R_{el}} \Delta V_R$$

Capacitance

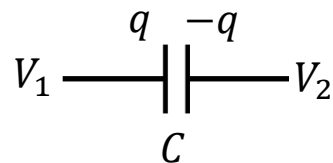


$$q = -C(V_2 - V_1) \quad i = \frac{dq}{dt}$$


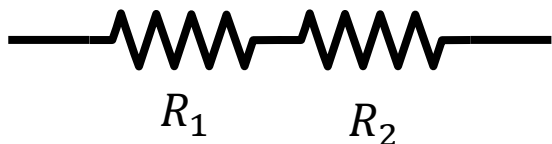
$$i = -C \frac{d}{dt} (V_2 - V_1) = -C \frac{d\Delta V_C}{dt}$$



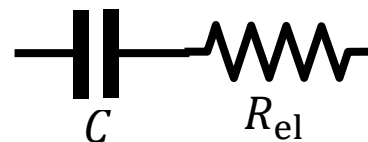
$$i = -C \frac{d}{dt} (\Delta V_C) \quad i = -\frac{1}{R_{el}} (\Delta V_R)$$



Charging of a Capacitor

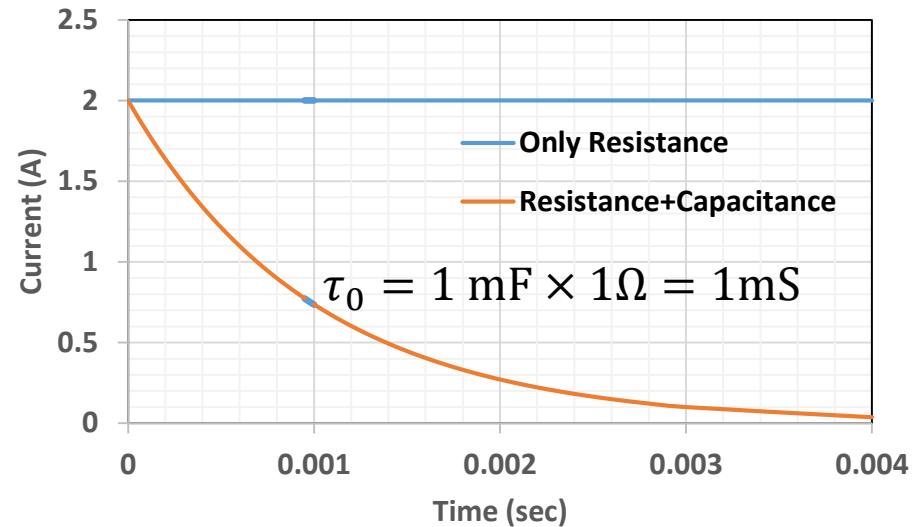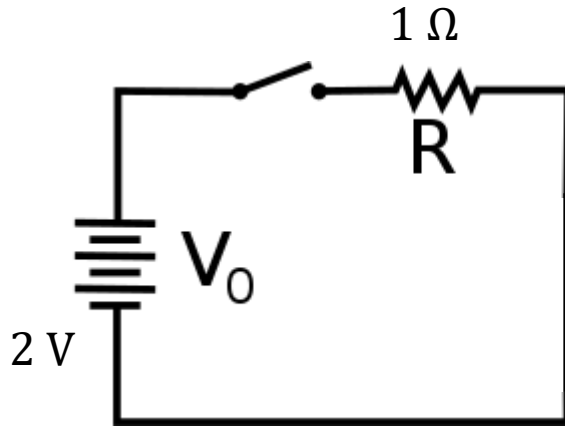

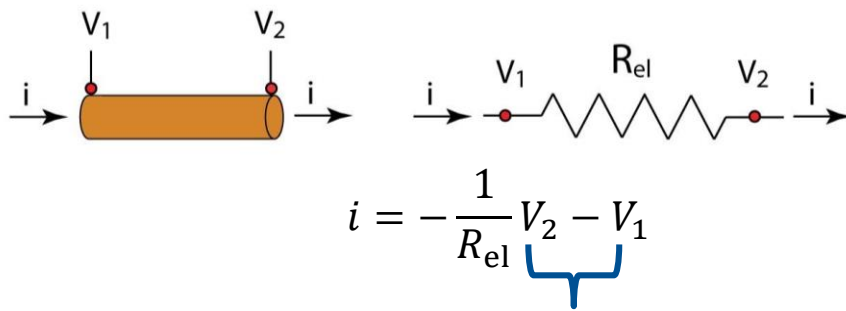How can I compare Capacitor and Resistor?
 For a given potential drop: Resistor gives you constant current but capacitor gives you decreasing current.



$$i = -C \underbrace{\frac{d}{dt}(V_2 - V_1)}$$

If both of them are comparable or similar!!!!

Math for the rescue!



$$i = -\frac{1}{R_{\text{el}}} V_2 - V_1$$

$$i = -C \frac{d}{dt} (V_2 - V_1)$$

If both of them are comparable or similar!!!!

$$\text{If } V_2 - V_1 = V_0 \sin(\omega t)$$

$$\frac{d}{dt} (V_2 - V_1) = \omega V_0 \sin(\omega t + 90^\circ)$$

$$i = -\left[\frac{1}{R_{\text{el}}}\right] \sin(\omega t + 0)$$

$$i = -[C\omega V_0] \sin(\omega t + 90^\circ)$$

Also provide additional nice properties like periodicity!!!!





Outline



- ☐ Motivation for EIS
 - ☐ Previous encounter
- ☐ Impedance (loosely defined)
 - ☐ Resistance
 - ☐ Capacitance (double layer capacitance)
 - ☐ Inductance (not covered)
- ☒ Impedance: definition
- ☐ Examples

Lets Define Impedance!

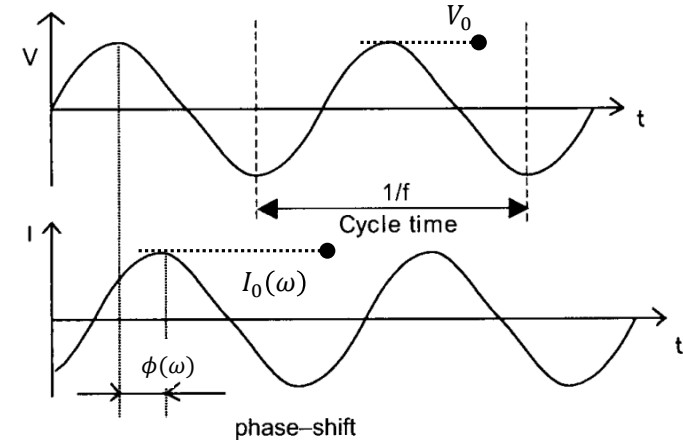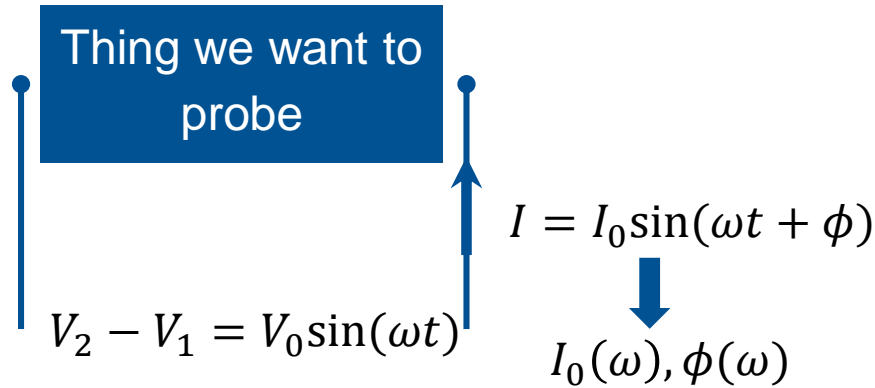

❑ Definition 1 (defined in many places)

$$Z = \frac{\Delta V}{I} = \frac{V_0 \sin(\omega t)}{I_0 \sin(\omega t + \phi)}$$

WRONG

Right Way to Define Z = ratio of complex voltage to complex current!



$$\mathbf{V} = \text{Laplace}(V(t)),$$

$$\mathbf{I} = \text{Laplace}(I(t))$$

$$\mathbf{Z}(\omega) = \frac{\Delta \mathbf{V}}{\mathbf{I}} \neq f(t)$$

$$\mathbf{Z}(\omega) = \frac{V_0}{I_0} e^{j\phi}$$


$$\mathbf{Z}(\omega) = \frac{V_0}{I_0(\omega)} e^{j\phi(\omega)}$$

Sample Calculations?


$$\mathbf{Z}(\omega) = \frac{V_0}{I_0} e^{j\phi}$$



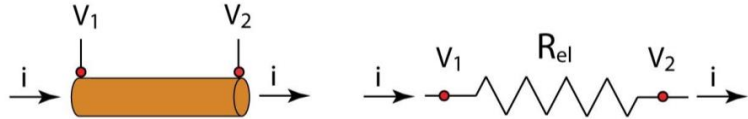- What is the advantage of defining impedance this way?
- Before we answer this, let's try to find out the impedance of a resistance and a capacitance!



$$i = -\frac{1}{R_{el}} V_2 - V_1$$

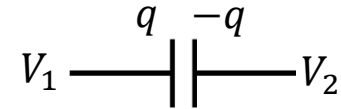

$$i = -C_{dl} \frac{d}{dt} (V_2 - V_1)$$

Complex Impedance (Laplace Transform) converts Differential Equations to Algebraic Expressions!


$$\mathbf{Z}(\omega) = \frac{V_0}{I_0} e^{j\phi} = \frac{V_0}{\left(\frac{1}{R_{el}} V_0\right)} e^{j \times 0}$$

$$\mathbf{Z}(\omega) = R_{el}$$


$$\mathbf{Z}(\omega) = \frac{V_0}{I_0} e^{j\phi} = \frac{V_0}{(V_0 C_{dl} \omega)} e^{j \times -\frac{\pi}{2}}$$

$$\mathbf{Z}(\omega) = \frac{-j}{C_{dl} \omega}$$

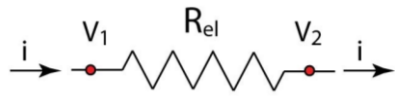Motivation for defining Impedance $z(\omega) = \frac{V_0}{I_0(\omega)} e^{j\phi(\omega)}$




$$Z_1 = R_{el}$$

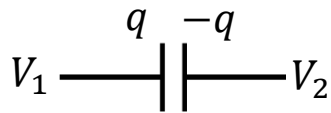

$$Z_2 = \frac{-j}{C\omega}$$



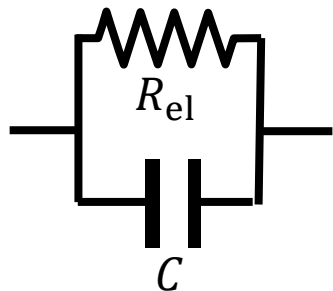Complex Impedance (Laplace Transform) allows you to use series parallel rules with any circuit element!



$$Z_4 = Z_1 || Z_2 = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

$$Z_4 = \frac{R_{el} \times \frac{-j}{C\omega}}{R_{el} + \frac{-j}{C\omega}} = \frac{-jR_{el}}{R_{el}C\omega - j}$$

$$\omega \rightarrow \infty \quad Z_4 \rightarrow 0 + 0j$$


$$\omega \rightarrow 0 \quad Z_4 \rightarrow R_{el} + 0j$$

$$\omega = \frac{1}{R_{el}C} \quad Z_4 \rightarrow -\frac{jR_{el}}{1-j} = \frac{R_{el}}{2} - \frac{jR_{el}}{2}$$


Nyquist Plots: Aspect Ratio



WRONG

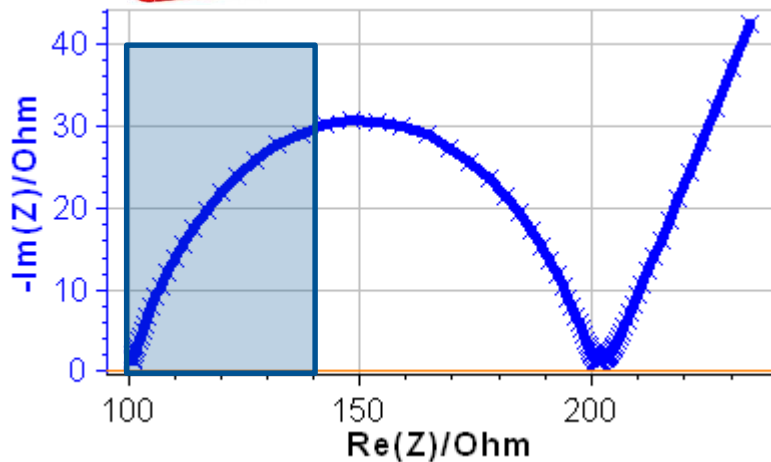

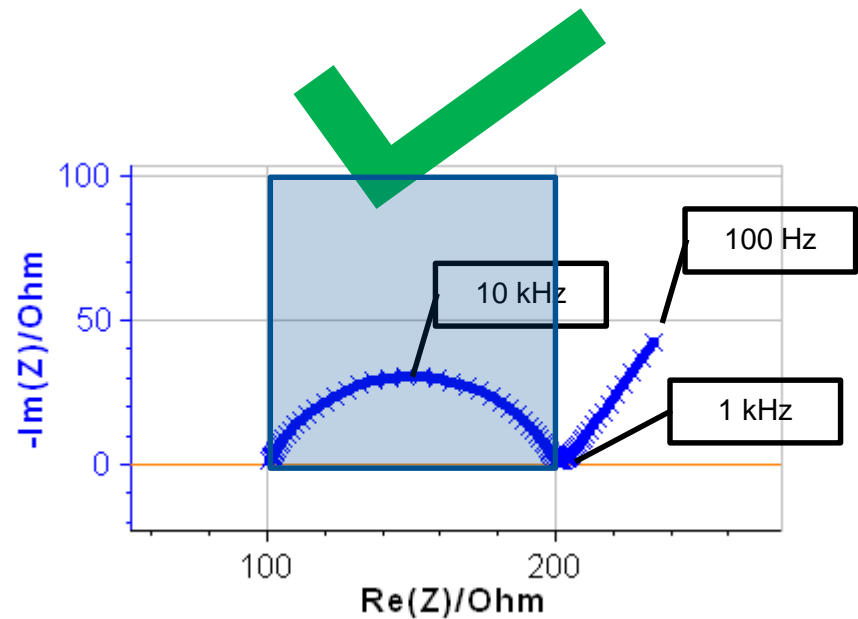Box of $40 \Omega \times 40 \Omega$ is a rectangle hence this is wrong



Box of $100 \Omega \times 100 \Omega$ is a square

A. Eisenstein

A. Eisenstein

L1 Ends



❑ Next Lecture:

❖ Transmission line model in EIS

Outline




- ☐ Motivation for EIS
 - ☐ Previous encounter
- ☐ Impedance (loosely defined)
 - ☐ Resistance
 - ☐ Capacitance (double layer capacitance)
 - ☐ Inductance (not covered)
- ☐ Impedance: definition
- ☒ Examples

System 1: Electrolytes with Non-Reacting Electrodes



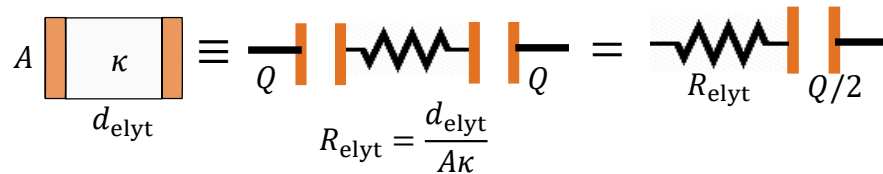1. PEM membrane (between two copper plates)



Membrane Follows Ohm's Law


$$\frac{\partial \phi}{\partial x} = - \frac{I}{\kappa_{\text{eff}}}$$

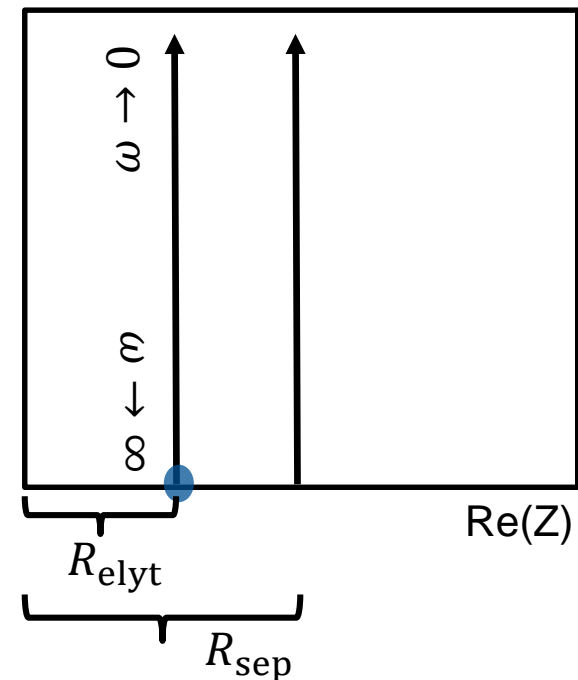2. Electrolyte soaked separator with Cu plates



$$\underbrace{\frac{\partial \phi}{\partial x} = - \frac{I}{\kappa_{\text{eff}}}}_{\text{Ohm's Law}} + \frac{2RT}{F} (\text{TDF})(1 - t_+) \frac{\partial c}{\partial x} \xrightarrow{0}$$

Since Cu plates \rightarrow No reaction \rightarrow No concentration Gradient




Leaky vs Conservative?

System 2: Electrolytes with Reacting Electrodes



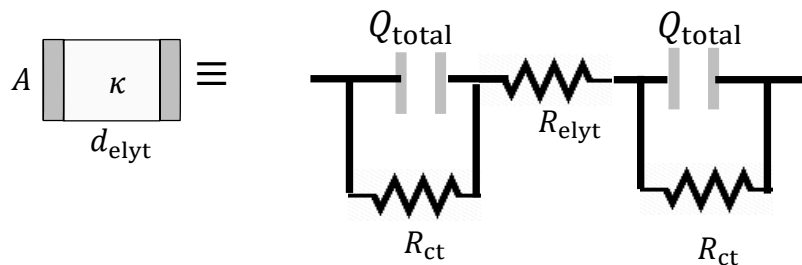1. PEM membrane (between two platinum **plates** in presence of H_2)



- Charge transfer process is a resistance because it follows ohm's law type expressions


$$j = j_0 \cdot \left\{ \exp \left[\frac{\alpha_a z F \eta}{RT} \right] - \exp \left[-\frac{\alpha_c z F \eta}{RT} \right] \right\}$$

- For small perturbation

$$j \left(\frac{RT}{nFj_0} \right) = (\eta)$$

R_{ct}

- Mathematically similar to Ohm's Law

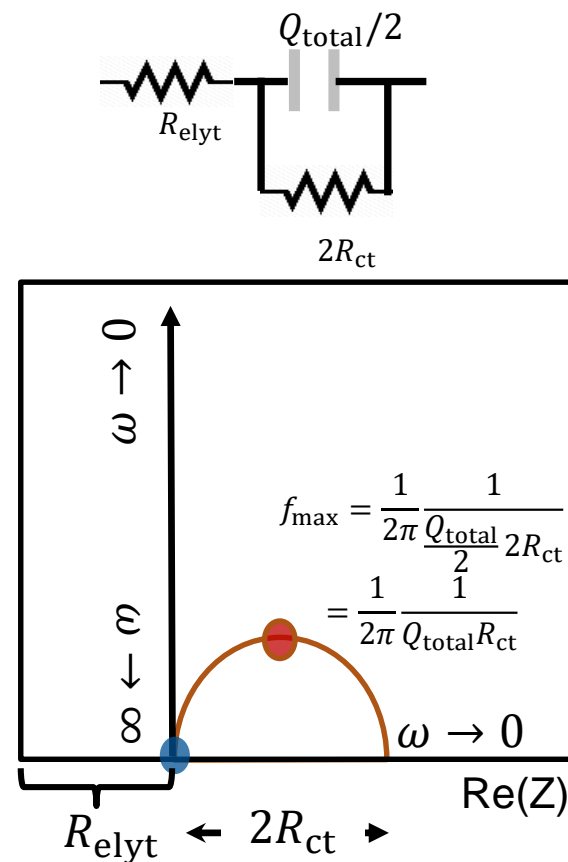

- What is Q_{total} ?
- Leaky vs Conservative?
- What happens to R_{ct} when Tafel Kinetics

Reference:



- ☐ Bard and Faulkner
- ☐ Fuller and Harb