

Quiz-3


Solution

Q1

To derive:

$$Z = \frac{R_{ion} \coth \sqrt{j\omega R_{ion} Q_{dl}}}{\sqrt{j\omega R_{ion} Q_{dl}}}$$

(a) Transmission line Model:

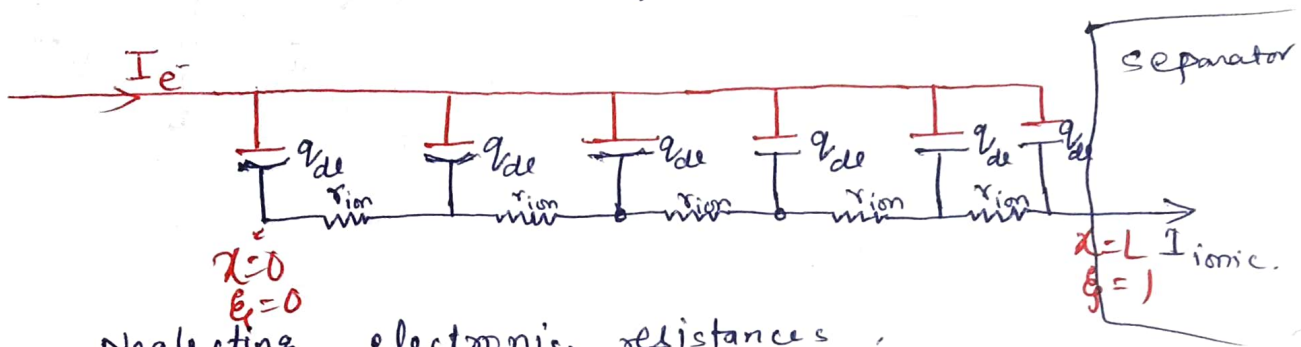

Neglecting electronic resistances,

$$\sum q_{dl} = Q_{dl}$$

$$\sum r_{ion} = R_{ion}$$

(b)

variable: potential across the thickness of electrode.

~~parameter~~

(c)

conservation law:

charge Balance:

Through a resistor, Ionic Current (In- Out) = change in Capacitive Current

$$-\frac{\partial}{\partial x} \left\{ -\kappa_{eff} \frac{\partial \phi}{\partial x} \right\} = i_{cdl} = C \frac{d\phi}{dt}$$

A/m^3

$$C \frac{d\phi}{dt} = \kappa_{eff} \frac{\partial^2 \phi}{\partial x^2}$$

$$\boxed{\frac{d\phi}{dt} = \frac{\kappa_{eff}}{C} \frac{\partial^2 \phi}{\partial x^2}}$$

Non dimensionalize

$$\text{Let } \xi = \frac{x}{L}$$

$$\therefore \frac{\partial \phi}{\partial t} = \frac{\kappa_{eff} A}{A \times C \times L \times L} \frac{\partial^2 \phi}{\partial \xi^2}$$

$$A \times C \times L = Q \rightarrow \text{Total capacitance of electrode}$$

$$\frac{\kappa_{eff} A}{L} = \frac{1}{R_{ion}}$$

$$\boxed{\frac{\partial \phi}{\partial t} = \frac{1}{R_{ion} Q} \frac{\partial^2 \phi}{\partial \xi^2}}$$

Boundary Conditions:

At $x=0$ (Near Current Collector), Ionic flux is zero.

$$-\kappa_{eff} \frac{\partial \phi}{\partial x} \bigg|_{x=0} = 0$$

①

$$-\kappa_{eff} \frac{\partial \phi}{\partial \xi} \bigg|_{\xi=0} = 0$$

③ At $x = L$ ($\xi = 1$) [Near Separator]
 $\Phi = 1$

④ Laplace Transform

$$L \left\{ \frac{\partial \Phi}{\partial t} \right\} = \frac{1}{R_{ion} Q} \frac{\partial^2 \Phi}{\partial \xi^2}$$

$$s \Phi = \frac{1}{R_{ion} Q} \frac{d^2 \Phi}{d \xi^2}$$

$$\frac{d^2 \Phi}{d \xi^2} = R_{ion} Q s \Phi$$

$$\frac{d^2 \Phi}{d \xi^2} = s^2 \Phi \quad [s^2 = R_{ion} Q s]$$

$$\Phi = c_1 \cosh[s \xi] + c_2 \sinh[s \xi]$$

∵ $\left. \frac{d\Phi}{d\xi} \right|_{\xi=0} = 0 \Rightarrow \boxed{c_2 = 0}$

$\Phi = 1$ @ $\xi = 1$

$$1 = c_1 \cosh[s]$$

$$c_1 = \frac{1}{\cosh[s]}$$

$$\therefore \Phi = \frac{\cosh[s \xi]}{\cosh[s]} \rightarrow \Phi \text{ in Laplace domain}$$

current in
laplace domain,

$$I = \frac{\epsilon A K_{eff}}{L} \frac{d\Phi}{d\xi}$$

(e) $Z = \left. \frac{\Phi}{I} \right|_{\xi=1}$ (in laplace domain)

(f) $Z = \left. \frac{\cosh[s\xi]}{\frac{A K_{eff}}{L} \frac{d\Phi}{d\xi}} \right|_{\xi=1}$

$Z = \frac{R_{ion}}{s} \cosh$

$\frac{A K_{eff}}{L} \frac{d\Phi}{d\xi} = s \cdot \frac{A K_{eff}}{L} \frac{\sinh[s\xi]}{\cosh[s]}$

$\therefore Z = \frac{R_{ion} \cosh[s]}{s}$

$\left\{ \because \frac{L}{A K_{eff}} = R_{ion} \right.$


$s = \sqrt{R_{ion} Q \beta} \quad \& \quad \beta = i\omega$

$s = \sqrt{R_{ion} Q \cdot i\omega}$


$Z = \frac{R_{ion} \cosh \sqrt{i\omega R_{ion} Q_{ac}}}{\sqrt{i\omega R_{ion} Q_{ac}}}$

g)
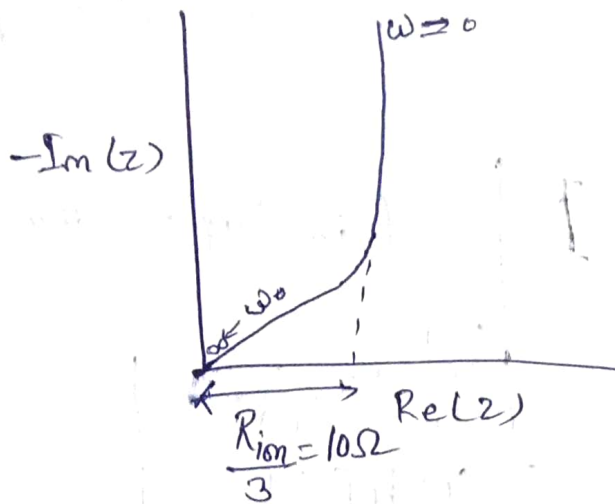
$$R_{ion} = 30 \Omega, \quad Q_{dl} = 1 \text{ mF}$$



h)

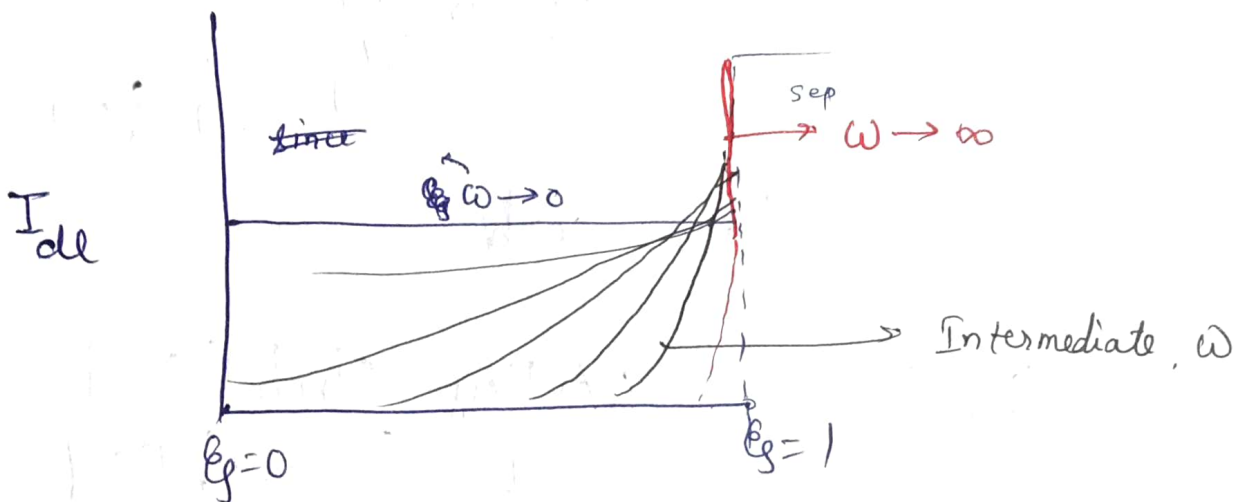

Since At $\omega \rightarrow 0$, current will flow equally from all the branches, therefore a flat line at $\omega \rightarrow 0$.

At $\omega \rightarrow \infty$, current will flow through the branch near separator only. Therefore huge current at near separator side at $\omega \rightarrow \infty$.

As ω decreases from ∞ , current will utilize more and more electrode part from separator side.


②

$$i = C \frac{dV}{dt} = C \cdot v, \quad C = 10 \text{ mF}$$

$$\text{At } v = 10 \frac{\text{mV}}{\text{s}}, \quad i = 100 \frac{\mu\text{A}}{\text{s}}$$

$$\text{At } v = 50 \frac{\text{mV}}{\text{s}}, \quad i = 500 \mu\text{A}$$
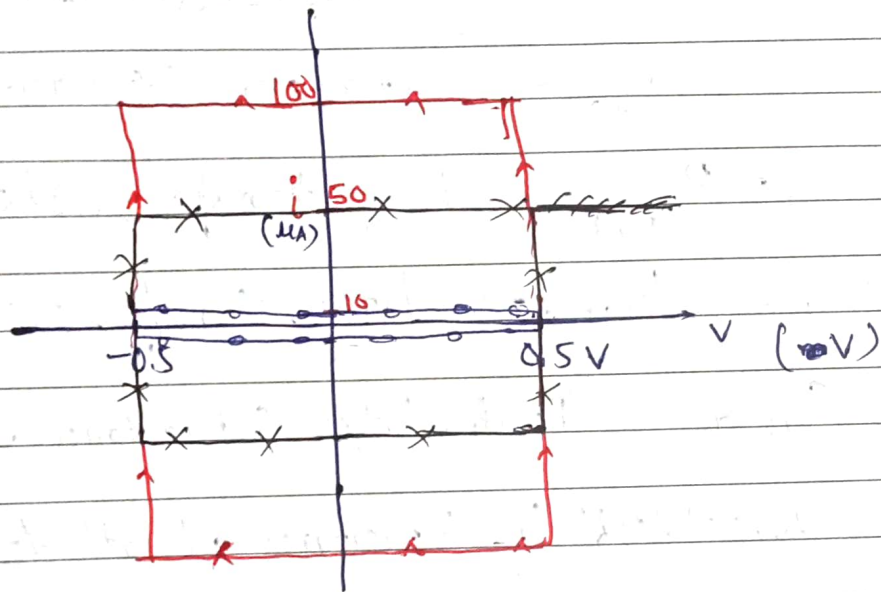
$$\text{At } v = 100 \frac{\text{mV}}{\text{s}}, \quad i = 1000 \frac{\mu\text{A}}{\text{s}}$$




③

$$i_R = \frac{v}{R} = 1$$

$$i_C = C \cdot v$$


1 mF

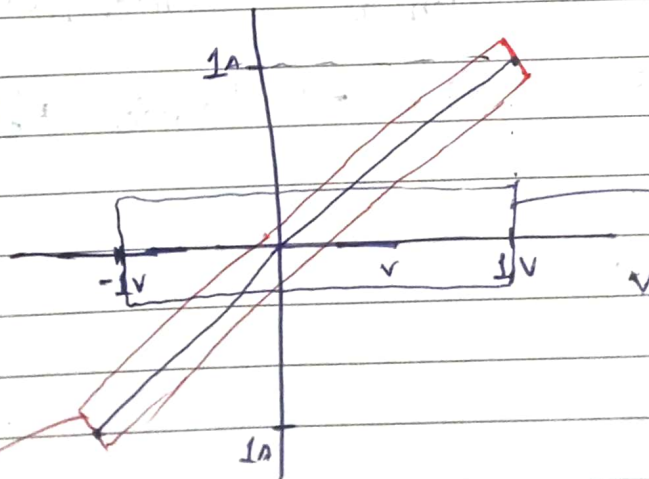

pure capacitor
i values will
depend on v

Resultant, R & C in parallel.

(4)

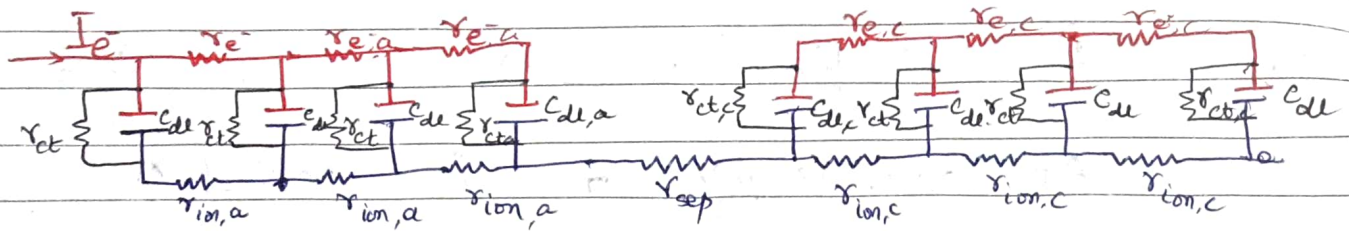

$R_{e,a} = \sum r_{e,a} \rightarrow$ electronic resistance through Anode

$R_{e,c} = \sum r_{e,c} \rightarrow$ electrode resistance in Cathode

$r_{sep} \rightarrow$ separator resistance

$\sum r_{ct,a} = R_{ct,a} \rightarrow$ charge transfer resistance of Anode

$\sum r_{ct,c} = R_{ct,c} \rightarrow$ Charge Transfer resistance of Cathode

$C_{dl,a} \rightarrow$ Double layer capacitance at Anode-electrolyte interface

$C_{dl,c} \rightarrow$ Double layer capacitance at Cathode electrolyte interface

$\sum r_{ion,a} = R_{ion,a} \rightarrow$ Ionic Resistance of Anode

$\sum r_{ion,c} = R_{ion,c} \rightarrow$ Ionic Resistance of Cathode

⑤ Single Particle Ass Model Assumption →

- ① NO conc^n gradient in electrolyte
- ② All the particles are assumed to be spherical and particle size is same.
- ③ Uniform current distribution throughout the electrode.
- ④ Each electrode can be represented as single particle.
- ⑤ Uniform flux on the surface of particle.

⑥

